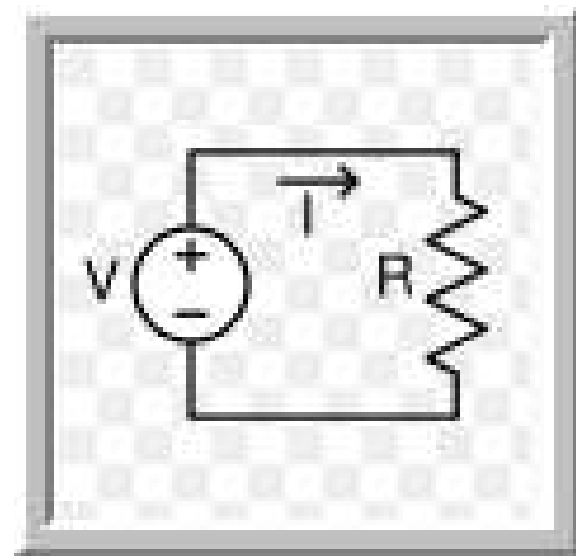


# Ohm's Law

- Ohm's law states that, in an electrical circuit, the current passing through most materials is directly proportional to the potential difference applied across them.



# 3-1—3-3: Ohm's Law Formulas

- There are three forms of Ohm's Law:
  - $I = V/R$
  - $V = IR$
  - $R = V/I$
- where:
  - $I$  = Current
  - $V$  = Voltage
  - $R$  = Resistance

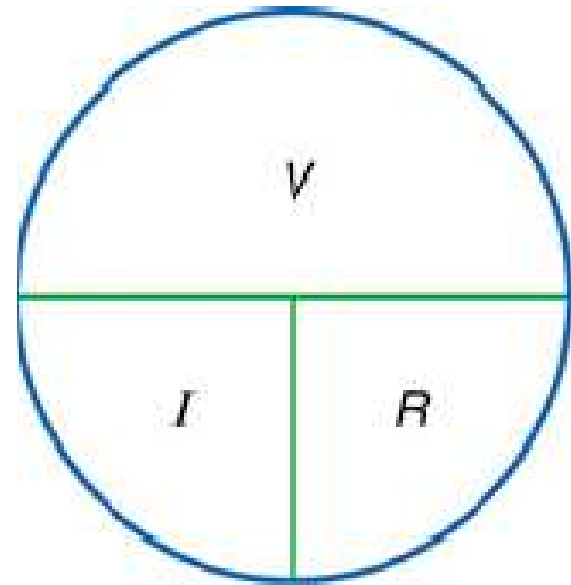


Fig. 3-4: A circle diagram to help in memorizing the Ohm's Law formulas  $V = IR$ ,  $I = V/R$ , and  $R = V/I$ . The  $V$  is always at the top.

# 3-1: The Current $I = V/R$

- $I = V/R$
- In practical units, this law may be stated as:
  - amperes = volts / ohms

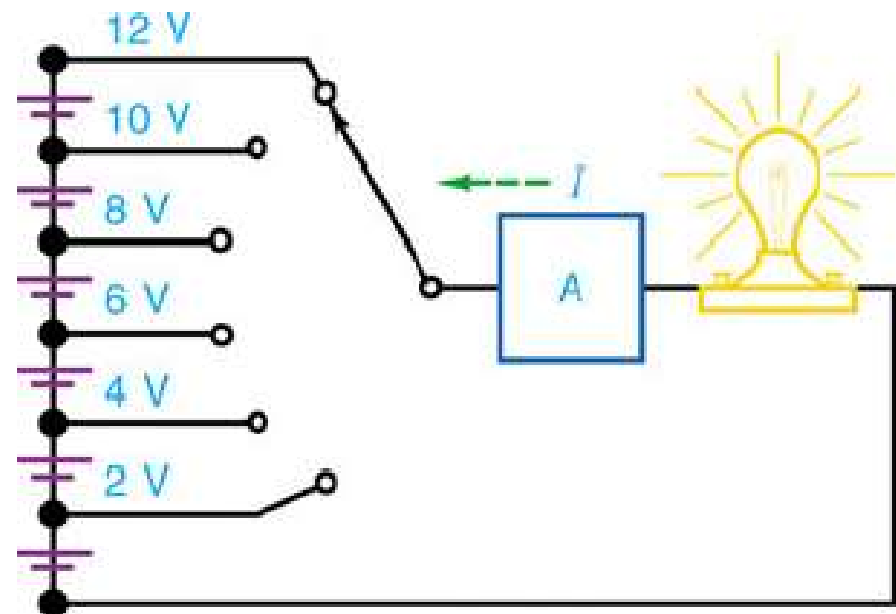






Fig. 3-1: Increasing the applied voltage  $V$  produces more current  $I$  to light the bulb with more intensity.

## 3-4: Practical Units

- The three forms of Ohm's law can be used to define the practical units of current, voltage, and resistance:
  - 1 ampere = 1 volt / 1 ohm
  - 1 volt = 1 ampere  $\times$  1 ohm
  - 1 ohm = 1 volt / 1 ampere

## 3-4: Practical Units

Applying Ohm's Law

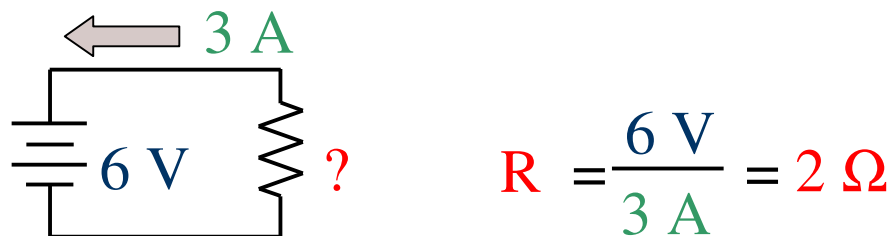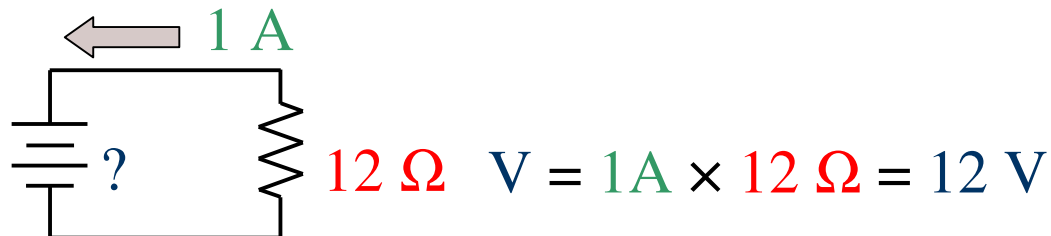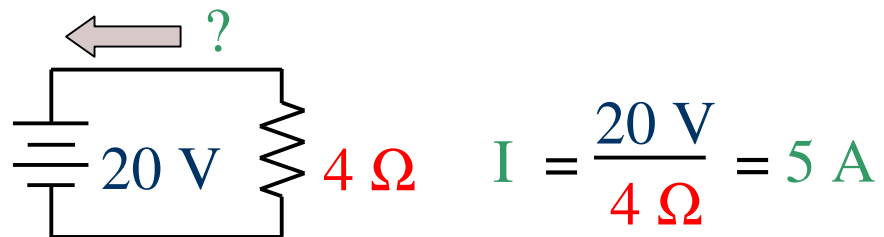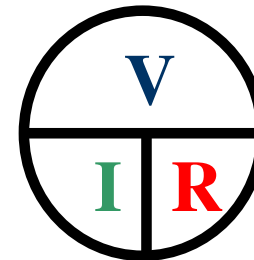

# Problem

- Solve for the resistance,  $R$ , when  $V$  and  $I$  are known
  - a.  $V = 14 \text{ V}$ ,  $I = 2 \text{ A}$ ,  $R = ?$
  - b.  $V = 25 \text{ V}$ ,  $I = 5 \text{ A}$ ,  $R = ?$
  - c.  $V = 6 \text{ V}$ ,  $I = 1.5 \text{ A}$ ,  $R = ?$
  - d.  $V = 24 \text{ V}$ ,  $I = 4 \text{ A}$ ,  $R = ?$

## 3-5: Multiple and Submultiple Units

- Units of Voltage

- The basic unit of voltage is the **volt (V)**.

- Multiple units of voltage are:

- **kilovolt (kV)**

- 1 thousand volts or  $10^3$  V

- **megavolt (MV)**

- 1 million volts or  $10^6$  V

- Submultiple units of voltage are:

- **millivolt (mV)**

- 1-thousandth of a volt or  $10^{-3}$  V

- **microvolt ( $\mu$ V)**

- 1-millionth of a volt or  $10^{-6}$  V

## 3-5: Multiple and Submultiple Units

### ■ Units of Current

- The basic unit of current is the **ampere (A)**.
- Submultiple units of current are:
  - **milliampere (mA)**  
1-thousandth of an ampere or  $10^{-3}$  A
  - **microampere ( $\mu$ A)**  
1-millionth of an ampere or  $10^{-6}$  A



## 3-5: Multiple and Submultiple Units

- Units of Resistance
  - The basic unit of resistance is the **Ohm ( $\Omega$ )**.
  - Multiple units of resistance are:
    - **kilohm ( $k\Omega$ )**  
1 thousand ohms or  $10^3 \Omega$
    - **Megohm ( $M\Omega$ )**  
1 million ohms or  $10^6 \Omega$

# Problem

- How much is the current,  $I$ , in a  $470\text{-k}\Omega$  resistor if its voltage is  $23.5\text{ V}$ ?
- How much voltage will be dropped across a  $40\text{ k}\Omega$  resistance whose current is  $250\text{ }\mu\text{A}$ ?